

## 1 Lab 1A:

## 1.1 VHDL Code for 1 Bit Adder

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- asynchronous two bit binary adder with output result as binary addition
-- with overflow input and output.

entity full_adder_1bit is
    Port (
        addend0    : in  STD_LOGIC; -- 1 bit input to be added
        addend1    : in  STD_LOGIC; -- 1 bit input to be added
        carry_in   : in  STD_LOGIC; -- carry in 1 or 0 to be added to addend1 and
                                   -- addend 0
        sum        : out STD_LOGIC; -- result of addend0, addend1 and carry in
                                   -- all summed
        carry_out  : out STD_LOGIC); -- carry_out 1 if sum overflows
end full_adder_1bit;

architecture Behavioral_1bit of full_adder_1bit is

    signal G      : STD_Loic;
    signal P      : STD_Loic;
    signal Cprop  : STD_Loic;

begin
    G      <= addend0 and addend1;
    P      <= addend0 xor addend1;
    Cprop  <= P and carry_in;

    carry_out <= Cprop or G;
    sum      <= P xor Carry_in;

end Behavioral_1bit;
```

## 1.2 Testbench Code for 1 Bit Adder

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity full_adder_1bit_tb is
end full_adder_1bit_tb;

architecture Behavioral of full_adder_1bit_tb is

    signal addend0: STD_LOGIC;
    signal addend1: STD_LOGIC;
    signal carry_in: STD_LOGIC;

    signal sum: STD_LOGIC;
    signal carry_out: STD_LOGIC;

begin
    UUT: entity work.full_adder_1bit
        PORT MAP (
            addend0 => addend0,
            addend1 => addend1,
            carry_in => carry_in,
            sum => sum,
            carry_out => carry_out);

    Test : process
    begin

        -- tests each of the 8 different input variations to the entity
        -- the inputs represented in binary MSB(addend0,addend1,carry_in)LSB
        --begin at 000 and increment e.g. 000->001-> 010..... carrying on to targets
        -- input value 111

        -- wait 100 ns for global reset to finish
        wait for 100 ns;

        addend0 <= '0';
        addend1 <= '0';
        carry_in <= '0';
        wait for 10ns;

        addend0 <= '0';
        addend1 <= '0';
        carry_in <= '1';
        wait for 10ns;

        addend0 <= '0';
        addend1 <= '1';
        carry_in <= '0';
        wait for 10ns;

        addend0 <= '0';
        addend1 <= '1';
        carry_in <= '1';
        wait for 10ns;
```

```

addend0 <= '1';
addend1 <= '0';
carry_in <= '0';
wait for 10ns;


addend0 <= '1';
addend1 <= '0';
carry_in <= '1';
wait for 10ns;

addend0 <= '1';
addend1 <= '1';
carry_in <= '0';
wait for 10ns;

addend0 <= '1';
addend1 <= '1';
carry_in <= '1';

```

### 1.3 Simulation Results

 

### 1.4 RTL Component Statistics

-----  
Start RTL Component Statistics  
-----

Detailed RTL Component Info :

+---XORs :  
2 Input          1 Bit          XORs := 2

-----  
Finished RTL Component Statistics  
-----

## 1.5 Pin Assignments

```
set_property PACKAGE_PIN F22 [get_ports {carry_in}]
set_property IOSTANDARD LVCMOS18 [get_ports {carry_in}]
set_property PACKAGE_PIN G22 [get_ports {addend0}]
set_property IOSTANDARD LVCMOS18 [get_ports {addend0}]
set_property PACKAGE_PIN H22 [get_ports {addend1}]
set_property IOSTANDARD LVCMOS18 [get_ports {addend1}]
set_property PACKAGE_PIN T22 [get_ports {sum}]
set_property IOSTANDARD LVCMOS18 [get_ports {sum}]
set_property PACKAGE_PIN T21 [get_ports {carry_out}]
set_property IOSTANDARD LVCMOS18 [get_ports {carry_out}]
```

## 2 Lab 1B

## 2.1 VHDL Code for 4 Bit Adder

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Four bit binary adder for the addition of 2 four bit signals and a four bit output value
--The Entity contains 4 iterations of a two input 1 bit adder with carry in and carry out
-- bits for overflow carrying over functionality.

entity full_adder_4bit is
    Port (
        First_Addend : in  STD_LOGIC_VECTOR (3 downto 0); -- 4 bit input to be added
        Second_Addend : in  STD_LOGIC_VECTOR (3 downto 0); -- 4 bit input to be added
        carry_in      : in  STD_LOGIC;                    -- carry in 1 bit passed from previous
                                                         -- carryout overflow
        Sum           : out STD_LOGIC_VECTOR (3 downto 0); -- result of addition of First_Addend,
                                                         -- Second_Addend & carry in check
        carry_out     : out STD_LOGIC);                  -- over flow result from addition of
                                                         -- First_Addend & Second_Addend
end full_adder_4bit;

architecture Behavioral_4bit of full_adder_4bit is
    -- naming conventions : Internal-Origin-Destination
    -- int: internal wire
    -- Fa: full adder
    -- following number refers to the full adder number
    -- Co refers to Carry out
    -- Ci refers to Carry in
    signal int_Fa0Co_Fa1Ci : STD_LogiC; -- function is to connect the Carryout of adder 0 to the carry in 1
    signal int_Fa1Co_Fa2Ci : STD_LogiC; -- function is to connect the Carryout of adder 1 to the carry in 2
    signal int_Fa2Co_Fa3Ci : STD_LogiC; -- function is to connect the Carryout of adder 2 to the carry in 3

begin

    -- 1 bit adder 0
    full_adder_1bit_0: entity work.full_adder_1bit
    port map (
        addend0  => First_Addend(0),    -- input of 4 bit vector First_Addend bit '0' connects to 1 bit adder0 addend0
        addend1  => Second_Addend(0),   -- input of 4 bit vector Second_Addend bit '0' connects to 1 bit adder0 addend1
        sum      => sum(0),              -- output of 1 bit adder 0 sum connects to bit vector sum bit '0'
        carry_in => carry_in,            -- 1 bit carry in signal directly connect to adder 0 carry in
        carry_out => int_Fa0Co_Fa1Ci);   -- carry out connects to signal "int_Fa0Co_Fa1Ci" to connect to adder 1
                                         -- carry in input

    -- 1 bit adder 1
    full_adder_1bit_1: entity work.full_adder_1bit
    port map (
        addend0  => First_Addend(1),    -- input of 4 bit vector First_Addend bit '1' connects to 1 bit adder1
                                         -- addend0
        addend1  => Second_Addend(1),   -- input of 4 bit vector Second_Addend bit '1' connects to 1 bit adder1
                                         -- addend1
        sum      => sum(1),              -- output of 1 bit adder 1 sum connects to bit vector sum bit '1'
        carry_in => int_Fa0Co_Fa1Ci,    -- 1 bit carry in connects to signal "int_Fa0Co_Fa1Ci" from adder 0 carry
                                         -- out
        carry_out => int_Fa1Co_Fa2Ci);   -- carry out connects to signal "int_Fa1Co_Fa2Ci" to connect to adder 2
                                         -- carry in input

    -- 1 bit adder 2
    full_adder_1bit_2: entity work.full_adder_1bit
    port map (
        addend0  => First_Addend(2),    -- input of 4 bit vector First_Addend bit '2' connects to 1 bit adder2
                                         -- --addend0
        addend1  => Second_Addend(2),   -- input of 4 bit vector Second_Addend bit '2' connects to 1 bit adder2
                                         -- -- addend1
        sum      => sum(2),              -- output of 1 bit adder 2 sum connects to bit vector sum bit '2'

```

```
carry_in => int_Fa1Co_Fa2Ci,    -- 1 bit carry in connects to signal "int_Fa1Co_Fa2Ci" from adder 1 carry
                                -- out
carry_out => int_Fa2Co_Fa3Ci);  -- carry out connects to signal "int_Fa2Co_Fa3Ci" to connect to adder 3
                                carry in input

-- 1 bit adder 3
full_adder_1bit_3: entity work.full_adder_1bit
port map (
addend0  => First_Addend(3),    -- input of 4 bit vector First_Addend bit '3' connects to 1 bit adder3 addend0
addend1  => Second_Addend(3),   -- input of 4 bit vector Second_Addend bit '3' connects to 1 bit adder3 addend1
sum      => sum(3),             -- output of 1 bit adder 3 sum connects to bit vector sum bit '3'
carry_in => int_Fa2Co_Fa3Ci,    -- 1 bit carry in connects to signal "int_Fa2Co_Fa3Ci" from adder 2 carry out
carry_out => carry_out);        -- carry out connects directly to output port carry_out
```

## 2.2 Testbench Code for 4 Bit Adder

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity full_adder_4bit_tb is
end full_adder_4bit_tb;

architecture Behavioral_4bit of full_adder_4bit_tb is
signal First_Addend   : STD_LOGIC_VECTOR (3 downto 0);
signal Second_Addend  : STD_LOGIC_VECTOR (3 downto 0);
signal carry_in       : STD_LOGIC;

signal Sum            : STD_LOGIC_VECTOR (3 downto 0);
signal carry_out      : STD_LOGIC;

begin

UUT: entity work.full_adder_4bit
    PORT MAP (First_Addend => First_Addend,
              Second_Addend => Second_Addend,
              carry_in      => carry_in,
              Sum           => Sum,
              carry_out     => carry_out);

TEST : process
-- testing strategy:
-- test that the whole 4 bit adder works
--correcty for numbers including and below 15

--test the carry_in and carry_out connection
--between each 1 bit counter

--test the final carry out which makes anwser
--given the remainder of whatever number it is minus 15

begin
-- wait 100 ns for global reset tot finish
wait for 100 ns;
-- testing 4 bit adder works correctly
--for output sum"0000" carry_out'0'
First_Addend  <= "0000";
Second_Addend <= "0000";
carry_in      <= '0';
wait for 10 ns;

--testing each adders inputs and result for both
-- check individual bits add together
--without over flow for output sum"1111" carry_out'0'
First_Addend  <= "0101";
Second_Addend <= "1010";
carry_in      <= '0';
wait for 10 ns;

-- check individual bits add together
--without over flow for output sum"1111" carry_out'0'
First_Addend  <= "1010";
Second_Addend <= "0101";
carry_in      <= '0';
wait for 10 ns;

```

```
--testing each 1 bit adder carryout with the next carry in
-- Check Carry_in for full_adder_1bit_1
--for output sum"0010" carry_out'0'
First_Addend <= "0001";
Second_Addend <= "0001";
carry_in <= '0';
wait for 10 ns;

-- Check Carry_in for full_adder_1bit_2
--for output sum"0100" carry_out'0'
First_Addend <= "0010";
Second_Addend <= "0010";
carry_in <= '0';
wait for 10 ns;

-- Check Carry_in for full_adder_1bit_3
--for output sum"1000" carry_out'0'
First_Addend <= "0100";
Second_Addend <= "0100";
carry_in <= '0';
wait for 10 ns;

-- Check Carry_out for full_adder_1bit_3
--for output sum"0000" carry_out'1'
First_Addend <= "1000";
Second_Addend <= "1000";
carry_in <= '0';
wait for 10 ns;

--for output cannot be used as to big output vector
--size for carry_out'1'
First_Addend <= "1000";
Second_Addend <= "1000";
carry_in <= '0';
wait for 10 ns;

--for output cannot be used as to big output vector
--size for carry_out'1'
First_Addend <= "0100";
Second_Addend <= "1100";
carry_in <= '0';
wait for 10 ns;


--for output cannot be used as to big output vector
--size for carry_out'1'
First_Addend <= "0111";
Second_Addend <= "1100";
carry_in <= '0';
wait for 10 ns;

wait; -- will wait forever
end process;

end Behavioral_4bit;
```



## 2.3 Simulation Results

 

## 2.4 RTL Component Statistics &amp; RTL Hierarchical Component Statistics

```
-----
Start RTL Component Statistics
-----
```

```
Detailed RTL Component Info :
```

```
+---XORs :
2 Input      1 Bit      XORs := 8
-----
```

```
Finished RTL Component Statistics
-----
```

```
Start RTL Hierarchical Component Statistics
-----
```

```
Hierarchical RTL Component report
```

```
Module full_adder_1bit
```

```
Detailed RTL Component Info :
```

```
+---XORs :
2 Input      1 Bit      XORs := 2
-----
```

```
Finished RTL Hierarchical Component Statistics
-----
```

## 3 Lab 2A

## 3.1 VHDL Code for 4-bit Counters

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
-- The Four_4bit_counters entity is made up of 4 individual counters that
--increment by one at the rising clock edge. They all count from 0 to 15
-- then role over back to zero again and continue incrementing.
-- the four different types of counters are:
--Synchronous reset and no enable
-- Asynchronous reset(clear) and no enable
-- Synchronous reset and enable
-- Aynchronous reset(clear) and enable
entity Four_4bit_counters is
Port (
clk : in STD_LOGIC;
rst : in STD_LOGIC;
en : in STD_LOGIC;

Sync_Reset_No_Enable : out UNSIGNED (3 downto 0);
Asyn_Reset_No_Enable : out UNSIGNED (3 downto 0);
Sync_Reset_Enable : out UNSIGNED (3 downto 0);
Asyn_Reset_Enable : out UNSIGNED (3 downto 0));
end Four_4bit_counters;

architecture Behavioral of Four_4bit_counters is
-- signals decelerations
--Each of these signals is used in its appropriate counter to
--increment the current value and connect to the corresponding 4 bit
--output port of the entity.
signal Sync_Reset_No_Enable_int : UNSIGNED(3 downto 0);
signal Asyn_Reset_No_Enable_int : UNSIGNED(3 downto 0);
signal Sync_Reset_Enable_int : UNSIGNED(3 downto 0);
signal Asyn_Reset_Enable_int : UNSIGNED(3 downto 0);
begin
--Synchronous reset and no enable
CNT_SYN_No_EN : process(clk)
begin
if(rising_edge(clk)) then
if (rst= '1') then
Sync_Reset_No_Enable_int <=(others => '0');
else
Sync_Reset_No_Enable_int <= (Sync_Reset_No_Enable_int +1);
end if;
end if;
end process CNT_SYN_No_EN;
Sync_Reset_No_Enable <= Sync_Reset_No_Enable_int;

-- Asynchronous reset(clear) and no enable
CNT_ASYNC_NO_EN : process(clk,rst)
begin
if (rst= '1') then
Asyn_Reset_No_Enable_int <=(others => '0');
else
if(rising_edge(clk)) then
Asyn_Reset_No_Enable_int <= (Asyn_Reset_No_Enable_int +1);
end if;
end if;
end process CNT_ASYNC_NO_EN;
Asyn_Reset_No_Enable <= Asyn_Reset_No_Enable_int;

```

```
-- Synchronous reset and enable
CNT_SYN_EN : process(clk)
begin
  if(rising_edge(clk)) then
    if (rst= '1') then
      Sync_Reset_Enable_int <=(others => '0');
    else
      if(en= '1') then
        Sync_Reset_Enable_int <= (Sync_Reset_Enable_int +1);
      end if;
    end if;
  end if;
end process CNT_SYN_EN;
Sync_Reset_Enable <= Sync_Reset_Enable_int;

-- Asynchronous reset(clear) and enable
CNT_ASYNC_EN : process(clk,rst)
begin
  if (rst= '1') then
    Asyn_Reset_Enable_int <=(others => '0');
  else
    if(rising_edge(clk)) then
      if(en= '1') then
        Asyn_Reset_Enable_int <= (Asyn_Reset_Enable_int +1);
      end if;
    end if;
  end if;
end process CNT_ASYNC_EN;
Asyn_Reset_Enable <= Asyn_Reset_Enable_int;

end Behavioral;
```

## 3.2 Testbench Code for 4-Bit Adder

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Four_4bit_counters_tb is
end Four_4bit_counters_tb;

architecture Behavioral of Four_4bit_counters_tb is

    signal clk : STD_LOGIC;
    signal rst : STD_LOGIC;
    signal en : STD_LOGIC;

    signal Sync_Reset_No_Enable: UNSIGNED(3 downto 0);
    signal Asyn_Reset_No_Enable: UNSIGNED(3 downto 0);
    signal Sync_Reset_Enable: UNSIGNED(3 downto 0);
    signal Asyn_Reset_Enable: UNSIGNED(3 downto 0);

    constant clk_period : time := 10ns;

begin

    UUT: entity work.Four_4bit_counters
        PORT MAP (clk => clk ,
                 rst => rst,
                 en => en,
                 Sync_Reset_No_Enable => Sync_Reset_No_Enable,
                 Asyn_Reset_No_Enable => Asyn_Reset_No_Enable,
                 Sync_Reset_Enable => Sync_Reset_Enable,
                 Asyn_Reset_Enable => Asyn_Reset_Enable);

    -- Clock process
    -- clock period set to 10ns, repeats forever
    clk_process : process
    begin
        clk <= '0';
        wait for clk_period/2;
        clk <= '1';
        wait for clk_period/2;
    end process;

    TEST : process
    -- testing process checks :
    -- counter outputs begin from zero at reset
    -- Synchronous reset counters reset output value to 0 at rising edge of clock
    -- Asynchronous reset counters reset output value to 0 at point reset signal is 1
    -- check that all counters count to 15 then roll over back to 0
    -- check that counters with enable signal only increment when enable is 1
    begin
        -- wait 100 ns for global reset to finish set by Xilinx
        wait for 100 ns;
    end process;
```

```

-- sets start time for changing input values on falling edge of clock
--this allows clear changes of outputs on rising edge that do not
-- interfere
wait until falling_edge(clk);

-- proves asynchronous resets work instantaneously and synchronous waits for clk
--rising edge
--wait for clk_period;
rst <= '1';
en <= '0';
wait for clk_period;

-- allowing counters without enable to increment
rst <= '0';
en <= '0';
wait for clk_period*2;

-- allow counters with enable to increment
wait until falling_edge(clk);
rst <= '0';
en <= '1';
wait for clk_period*2;
-- offset reset to prove asynchronous reset not on clk edge
wait for clk_period*0.3;


--reset values back to zero synchronous and asynchronous
rst <= '1';
en <= '0';
wait for clk_period;


--count increment until transiton off 15 to 0 in hex
rst <= '0';
en <= '1';
wait for clk_period*10;
wait;-- wait forever
end process;

end Behavioral;

```

### 3.3 Simulation Results

 

 

3.4 RTL Component Statistics

```
-----
Start RTL Component Statistics
-----
Detailed RTL Component Info :
+---Adders :
      2 Input      4 Bit      Adders := 4
+---Registers :
      4 Bit      Registers := 4
-----
Finished RTL Component Statistics
-----
```

## 4 Lab2B

## 4.1 VHDL Code for 0-99 Counter

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
--This Entity IS a 0-99 counter that outputs 2, 7 bit outputs to two 7
-- segment displays. The number increments by 1 each time the enable
--button is pressed at the clock signal and resets back to 0 when the
--reset button is pressed or the button is pressed or counter
--increments 99 by 1 all at clock signal.
-- the Entire entity uses 2 debouncers one for each buttons, enable and
reset.
-- It uses a singgle 0-99 counter and 2 4bit to 7 bit decoders.
entity Counter_0_to_99 is
    Port ( clk : in STD_LOGIC;
          rst : in STD_LOGIC;
          en : in STD_LOGIC;
          Units_7_seg : out STD_LOGIC_VECTOR (6 downto 0);
          -- output to the units 7 segment display
          Tens_7_seg : out STD_LOGIC_VECTOR (6 downto 0));
          -- output to the Tens 7 segment display
end Counter_0_to_99;

architecture Behavioral of Counter_0_to_99 is

    signal int_debounced_rst_sig : std_logic;
    signal int_debounced_en_sig : std_logic;

    signal Unit_4bit_seg: UNSIGNED(3 downto 0);
    -- 4 bit unit signal from 0-99 counter to decoder

    signal Tens_4bit_seg: UNSIGNED(3 downto 0);
    -- 4 bit tens signal from 0-99 counter to decoder
begin

COUNT_0_99: entity work.Count_to_99
port map (
    en => int_debounced_en_sig,    --debounced enable signal
    rst => int_debounced_rst_sig,  --debounced reset signal
    clk => clk,
    tens => Tens_4bit_seg,  --tens unit 4 bit output to decoder
    Unit => Unit_4bit_seg); -- unit 4 bit output to decoder

Enable_Debounce: entity work.Debouncer
port map (
    clk => clk,
    sig => en,                -- enable input to debouncer
    deb_sig => int_debounced_en_sig );-- debounced output enable signal

Reset_Debounce: entity work.Debouncer
port map (
    clk => clk,
    sig => rst ,              -- reset input to debouncer
    deb_sig => int_debounced_rst_sig ); -- debounced output reset signal

Unit_7_seg_disp: entity work.Decoder_7seg_Display
port map (
    Four_bit_input => Unit_4bit_seg ,
    Seven_bit_output => Units_7_seg );

```

```
Tens_7_seg_disp: entity work.Decoder_7seg_Display
port map (
Four_bit_input    => Tens_4bit_seg ,
Seven_bit_output => Tens_7_seg );
end Behavioral;
```



```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
-- This 0-99 counter increments by 1 at each pulse of the
--input debounced enable signal and at the clk edge.
-- It resets to zero when a debounced reset signal is
-- introduced and at the clk edge.
-- The entire counter is made up of 2 smaller counters each counting
--from 0-9 one for tens and one for units, the units increments by one
--upon the enable signal and clk rising edge. while the tens unit requires
-- the clk edge, the enable signal and the units counter value to be 9.
-- both tens and units counters have synchronous reset.
entity Count_to_99 is
    Port (

        clk : in STD_LOGIC;
        en : in STD_LOGIC;
        rst : in STD_LOGIC;

        Tens : out UNSIGNED (3 downto 0);
        Unit : out UNSIGNED (3 downto 0));
end Count_to_99;

architecture Behavioral of Count_to_99 is

    signal int_CNTunit: UNSIGNED(3 downto 0 ); -- units value to be incremented, reset,
                                                checked and connected to output
    signal int_CNTtens: UNSIGNED(3 downto 0 ); -- tens value to be incremented, reset,
                                                checked and connected to output

begin
    cnt_unit: process(clk)
    begin
        if(rising_edge(clk)) then
            if(rst= '1') then
                int_CNTunit <=(others => '0');
            else
                if (en= '1') then
                    if(int_CNTunit = 9) then -- eq. to (CNTunit = "1001")
                        int_CNTunit <=(others => '0');
                    else int_CNTunit <=(int_CNTunit+1);
                    end if;
                end if;
            end if;
        end if;
    end process cnt_unit;

    cnt_tens: process(clk)
    begin
        if(rising_edge(clk)) then
            if(rst= '1') then
                int_CNTtens <=(others => '0');
            else
                if (en = '1') and (int_CNTunit="1001") then -- checks debounced enable signal &
                                                            output of units is equal to 9
                    if(int_CNTtens = 9) then -- eq. to (CNTtens = "1001")
                        int_CNTtens <=(others => '0');
                    else int_CNTtens <=(int_CNTtens+1);
                    end if;
                end if;
            end if;
        end if;
    end process CNT_tens;

    --Output connections
    Unit <= int_CNTunit;
    Tens <= int_CNTtens;

end Behavioral;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Decoder_7seg_Display is
    Port ( Four_bit_input : in UNSIGNED(3 downto 0);
          Seven_bit_output : out STD_LOGIC_VECTOR (6 downto 0));
end Decoder_7seg_Display;

-- 7 segment decoder bit values of the 6 down to zero output
-- displayed below working top middle and moving clock wise
-- around and finishing in the centre
-- the bit order is 0 top middle horizontal
--                   1 top right vertical
--                   2 bottom right vertical
--                   3 bottom middle horizontal
--                   4 left bottom vertical
--                   5 top left vertical
--                   6 middle horizontal
--
--  |_|
--  |_|
--
-- 0 =          1 =
--    |_|        |_|
--
-- 2 =          3 =
--    |_|        |_|
--
-- 4 =          5 =
--    |_|        |_|
--
-- 6 =          7 =
--    |_|        |_|
--
-- 8 =          9 =
--    |_|        |_|
--
-- Error state =
--              |_|
--              |_|
architecture Behavioral of Decoder_7seg_Display is
begin
    with Four_bit_input select
    Seven_bit_output <= "0111111" when "0000", --0 dec= 63
                        "0000110" when "0001", --1 dec = 6
                        "1011011" when "0010", --2 dec = 91
                        "1001111" when "0011", --3 dec = 79
                        "1100110" when "0100", --4 dec =102
                        "1101101" when "0101", --5 dec =109
                        "1111101" when "0110", --6 dec =125
                        "0000111" when "0111", --7 dec = 7
                        "1111111" when "1000", --8 dec =127
                        "1101111" when "1001", --9 dec =111
                        "1111001" when others; --E dec =121 error state
end Behavioral;

```

## 4.2 Testbench Code for 0-99 Counter

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Counter_0_to_99_tb is

end Counter_0_to_99_tb;

architecture Behavioral of Counter_0_to_99_tb is

--input signals
signal clk : STD_LOGIC;
signal rst : STD_LOGIC;
signal en  : STD_LOGIC;

--output signals
signal Units_7_seg : STD_LOGIC_VECTOR (6 downto 0);
signal Tens_7_seg  : STD_LOGIC_VECTOR (6 downto 0);

--constants
constant clk_period : time := 10ns;

begin

UUT: entity work.Counter_0_to_99
    PORT MAP (clk => clk ,
              rst => rst,
              en  => en,
              Units_7_seg => Units_7_seg,
              Tens_7_seg => Tens_7_seg);

-- Clock process
clk_process :process
begin
    clk <= '0';
    wait for clk_period/2;
    clk <= '1';
    wait for clk_period/2;
end process;

--enable process to repeat simulating
-- an able button pressed
en_process :process
begin
wait until falling_edge(clk);
    en <= '0';
    wait for clk_period*5;
    en <= '1';
    wait for clk_period*5;
end process;

TEST : process
-- testing process tests:
-- synchronous tens and units increments with enable and clock

-- synchronous reset

-- reset counters values start from 0

--counters limited to 9 then back to 0
-- tens counter only increments when enable active, clk rising
--edge and units counter is 9

```

```

begin
-- wait 100 ns for global reset tot finish set by Xilinx
wait for 100 ns;

-- sets start time for changing input values on falling edge of clock
--this allows clear changes of outputs on rising edge that do not
-- interfere
wait until falling_edge(clk);
-- reset twice to clear out the unknown values within the registers
contained
-- within the debounce
rst <= '1';

-- multiples of clock period used to keep input changes on falling clk
edge
wait for clk_period*5;

rst <= '0';
wait for clk_period*5;

rst <= '1';
wait for clk_period*5;


rst <= '0';




wait for clk_period*5;



wait; --waits forever
end process;
end Behavioral;

```

### 4.3 Simulation Results

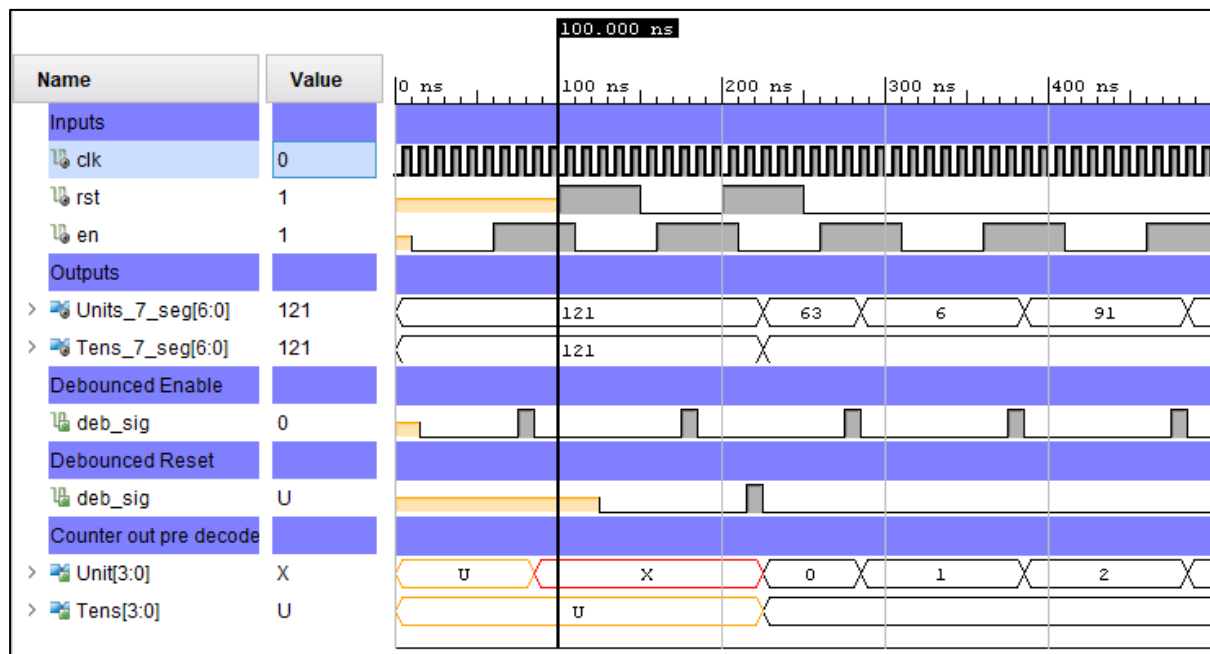

   

 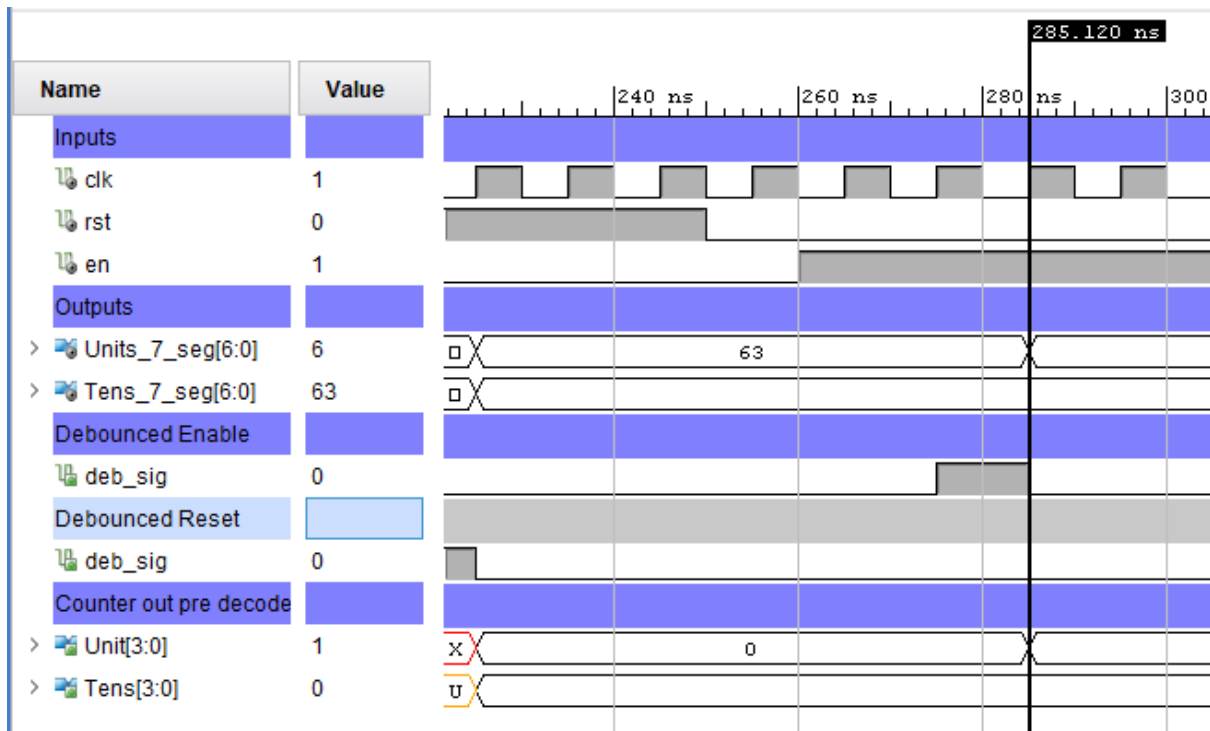

## RTL Component Statistics &amp; RTL Hierarchical Component Statistics

```

-----
Start RTL Component Statistics
-----
Detailed RTL Component Info :
+---Adders :
      2 Input      4 Bit      Adders := 2
+---Registers :
      4 Bit      Registers := 2
      1 Bit      Registers := 6
+---Muxes :
      2 Input      4 Bit      Muxes := 2
-----
Finished RTL Component Statistics
-----
Start RTL Hierarchical Component Statistics
-----
Hierarchical RTL Component report
Module Count_to_99
Detailed RTL Component Info :
+---Adders :
      2 Input      4 Bit      Adders := 2
+---Registers :
      4 Bit      Registers := 2
+---Muxes :
      2 Input      4 Bit      Muxes := 2
Module Debouncer
Detailed RTL Component Info :
+---Registers :
      1 Bit      Registers := 3
-----
Finished RTL Hierarchical Component Statistics
-----

```

The RTL Component statistics contain 2 adders which are implemented within the 0-99 adder as designed within the sequential logic. Two 4 bit registers are used to hold the current value within the counters system which makes sense as the values have to be incremented so the current value has to be remembered by the circuit. The 6 one bit registers are used within the debouncers each debouncer uses 3 registers that use 3 clock cycles worth of data with the 2 and gates and an inverted input to detect the falling edge of a button signal. The multiplexers are implemented as a comparator, if the select value equals 9 then the input changes to be equal to "0000" as defined in the if statements. It is strange that a single multiplexer per counter is used rather than a comparator as described in the sequential statement. This implementation makes sense as if a comparator was implemented instead more circuitry (probably a multiplexer) would be required to be implemented to complete the circuit as described.